

CPU Architecture

First Task

ALU Design with VHDL

Hanan Ribo

5/05/2020

Table of contents

1. Aim of Task1:.....	3
2. Assignment definition:	3
3. ALU high level design:.....	3
4. File based simulation of DUT:	5
5. Requirements:.....	6
6. Grading Policy	7

List of Figures

Figure 1: Overall DUT structure.....	3
--------------------------------------	---

List of Tables

Table 1 : ALU Op Codes	4
Table 2 : Status Bus	5

1. Aim of Task1:

- System design using concurrent and sequential logic principles using advanced Simulation methods (based on material given in LAB1 and LAB2 pre tasks).
- Preparation for Task2 – FPGA based design synthesis of this given ALU.
- Proper analysis and understanding of architecture design.

2. Assignment definition:

In this task you will design a basic registered ALU. The ALU will have following features (all the next sizes will be used with generic statement as given in tb.vhd):

- Two Input bus named A and B, width of 8-bit each as a default value
- Two Output buses named RES(HI,LO), width of 8-bit each as a default value
- One status bus output of 2-bit and an op-code input of 5-bit

You are required to design the whole system and make a test bench that tests all the system.

3. ALU high-level design:

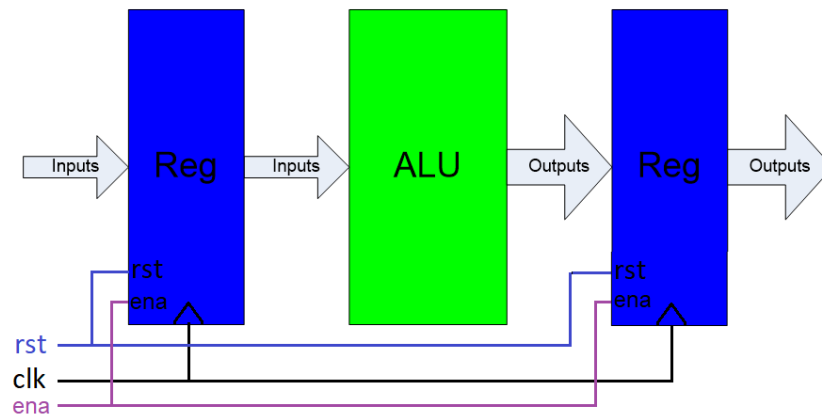


Figure 1: Overall DUT structure

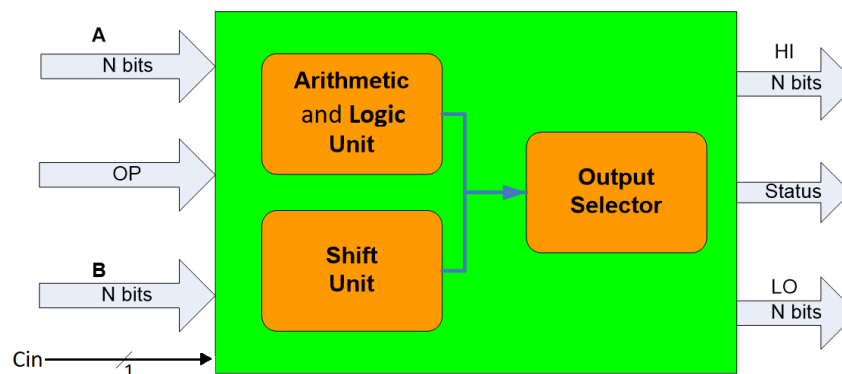


Figure 2: ALU structure

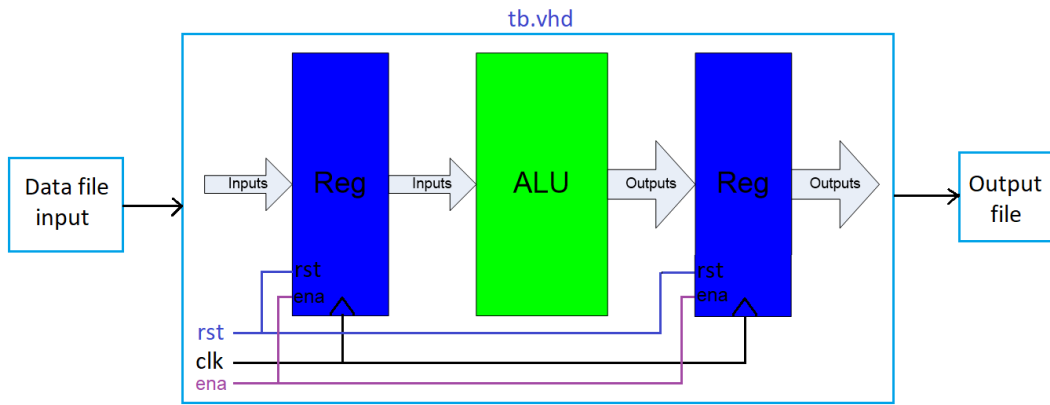


Figure 3: File based simulation of DUT

The following table describes all the available ALU Op codes and operation

Instruction	Opcode	Operation	Note
ADD	00001	$RES(HI,LO) = A + B$	As in lab1 requirement (see FAQ file)
SUB	00010	$RES(HI,LO) = A - B$	As in lab1 requirement (see FAQ file)
ADDC	00011	$RES(HI,LO) = A + B + Cin$	As in lab1 requirement (see FAQ file)
MULT	00100	$RES(HI,LO) = A * B$	Multiply two integer signed numbers (Result is $N*2$ bits)
MAC	00101	$ACC = ACC + A * B$ $RES(HI,LO) = ACC$	Multiply Accumulate (MAC is internal $N*2$ bits register) integer unsigned numbers
MAC_RST	00110	$MAC = 0$	Reset MAC
MAX	00111	$RES(0,LO) = \text{Max}(A,B)$	maximum between A and B
MIN	01000	$RES(0,LO) = \text{Min}(A,B)$	minimum between A and B
AND	01001	$RES(0,LO) = \text{AND}(A,B)$	Bitwise operation
OR	01010	$RES(0,LO) = \text{OR}(A,B)$	Bitwise operation
XOR	01011	$RES(0,LO) = \text{XOR}(A,B)$	Bitwise operation
RLA	01100	$RES(0,LO) = \text{rotation result}$	Rotate left A arithmetically B(2..0) times
RLC	01101	$RES(0,LO) = \text{rotation result}$	Rotate left A through carry B(2..0) times
RRA	01110	$RES(0,LO) = \text{rotation result}$	Rotate right A arithmetically B(2..0) times
RRC	01111	$RES(0,LO) = \text{rotation result}$	Rotate right A through carry B(2..0) times

Table 1 : ALU Op Codes

- Do **not** use additional arithmetic hardware for MAC operation; you must use the existing ADD/SUB and MULT modules.

 


Figure 4: MAC circuit

- The Status Bus of the ALU outputs is depicted in the next table:

Status Flag Name	Condition	Indicator (status ₁ , status ₀) ₂
C	Last OP produces carry	01
Z	Last OP result is zero	10
	else	00

Table 2 : Status Bus

- You are given the next two files that you must use in your project: **top.vhd**, **aux_package.vhd** (you can only add code to these files. you are not allowed to erase nothing).
- The ALU Top Level (without two wrapper registers) design must be Structural and contains the following entities:
 - ✓ Arithmetic and Logic Entity (For MULT, MAC, ADD/SUB, etc.)
 - ✓ Shift Entity (For shifts operations)
 - ✓ Output selector that formulates the output busses and status
- The Add/Sub module must be designed structurally (taken from LAB1).
- Other entities can be designed behaviorally, structurally, etc.

4. File based simulation of DUT:

- As depicted in figure 3, in order to simulate the DUT in systemly we use file based simulation.

- Input and Output files structure:

inputFile.txt - Notepad				outputFile.txt - Notepad			
File	Edit	Format	View	Help	File	Edit	Format
opcode	A	B	cin		RES(HI)	RES(HI)	Status

5. Requirements:

1. The design must be well commented.
2. Elaborated analysis and wave forms:
 - Remove irrelevant signals.
 - Zoom on regions of interest.
 - Draw clouds on the waveform with explanations of what is happening (Figure 4).
 - Change the waveform colors in ModelSim for clear documentation

(Tools->Edit Preferences->Wave Windows).

3. A ZIP file in the form of **id1_id2.zip** (where id1 and id2 are the identification number of the submitters, and id1 < id2) must be upload to Moodle only by id1 student. The ZIP file will contain:

Directory	Contains	Comments
VHDL	Project VHDL files	Only VHDL files, excluding test bench Note: your project files must be well compiled without errors as a basic condition before submission
TB	VHDL files that are used for test bench	Only one tb.vhd for the overall DUT
SIM	DO files of wave and list forms	Only for tb.vhd of the overall DUT
DOC	Project documentation	Readme.txt and pre2.pdf report file

Table 2: Directory Structure

 


Figure 3: Clouds over the waveform example

6. Grading Policy

Weight	Task	Description
10%	Documentation	The "clear" way in which you presented the requirements and the analysis and conclusions on the work you've done
90%	Analysis and Test	The correct analysis of the system (under the requirements)

Table 3 : Grading

Under the above policy, you will be also evaluated using common sense:

- Your files will be compiled and checked, the system must work.
 - Your design and architecture must be intelligent, minimal, effective and well organized.
4. **For a late submission the penalty is 2^{day}**